

Course Mechatronics System Modelling

Modelling a Solar Panel - Homework 1

Stefano Tonini 248413

Initialization


```
> restart:
with(plots):
with(LinearAlgebra):
with(GraphTheory):

interface(rtablesize=20):
plots[setcolors]("spring"):
c_set := ColorTools:-GetPalette("spring");

FONT_TYPE      := "Helvetica":
FONT_SIZE_LAB  := 14:
FONT_SIZE_TIT  := 18:
plots[setoptions](axes          = boxed,
                    size         = [800,200],
                    axis[2]      = [gridlines = [linestyle=dot]
],
                    legendstyle  = [location="top",font=
[FONT_TYPE,FONT_SIZE_LAB]],
                    labelfont    = [FONT_TYPE,FONT_SIZE_LAB],
                    axesfont     = [FONT_TYPE,FONT_SIZE_LAB],
                    titlefont    = [FONT_TYPE,bold,
FONT_SIZE_TIT],
                    captionfont  = [FONT_TYPE,italic,
FONT_SIZE_TIT],
                    labeldirections = [horizontal , vertical]
);
c_set := ⟨Palette Spring: Blue Rose YellowGreen BlueGreen Violet Cobalt Yellow PurpleRed (1.1)
GreenBlue PaleGreen Orange Purple Green SeaBlue PaleYellow PaleBlueGreen⟩
```

Battery Model

Ceraolo Battery Model

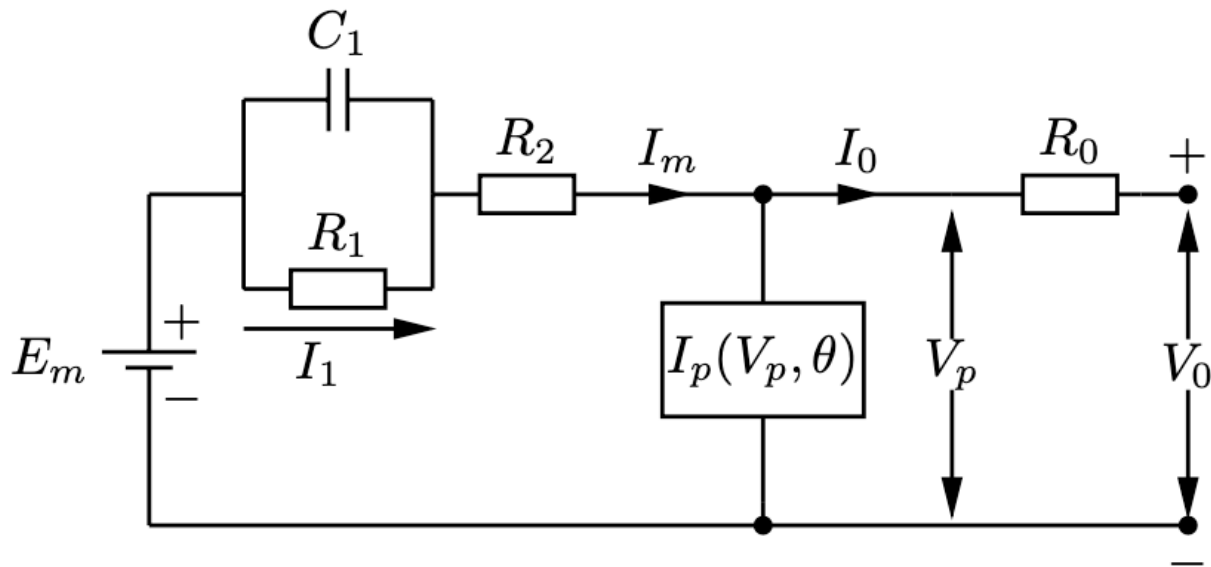

Parameters and variables:

Q_e extracted (or intake) charges.

- I_0 extracted current.
- I_1 current on the overvoltage branch.
- V_0 battery pins voltage.
- θ battery temperature.
- θ_a ambient temperature.

> # Define independent functions and variables

```
> MAXi0 := proc(Ic)
    max(0,Ic);
end proc;
```

```
> # Capacity
Capacity := proc(I_curr,theta) :
    local I__capacity := MAXi0(I_curr);
    (Cn/(Ac+(1-Ac)*(I__capacity/I_n)^delta))*((theta-theta__f)/
    (theta__n-theta__f))^epsilon;
end proc;
```

> # Parameters

```
params := [
    SOC = 1 - Q__e/Capacity(0,theta),
    DOC = 1 - Q__e/Capacity(I__1,theta),
    Em = Em0-KE*(273+theta)*(1-SOC),
```

```

R0 = R00*(1 + A0*(1 - SOC)),
R1 = -R10*log(DOC),
R2 = R20*( exp(A21(1 - SOC))/( 1 + exp (A22*I__m/In))))]

```

$$\begin{aligned}
 \text{params} := & \left[SOC = 1 - \frac{Q_e Ac}{C_n \left(\frac{\theta - \theta_f}{\theta_n - \theta_f} \right)^\epsilon}, DOC = 1 \right. \\
 & - \frac{Q_e \left(Ac + (1 - Ac) \left(\frac{\max(0, I_l)}{In} \right)^\delta \right)}{C_n \left(\frac{\theta - \theta_f}{\theta_n - \theta_f} \right)^\epsilon}, Em = Em0 - KE (273 + \theta) (1 \\
 & - SOC), R0 = R00 (1 + A0 (1 - SOC)), R1 = -R10 \ln(DOC), R2 \\
 & \left. = \frac{R20 e^{A21(1 - SOC)}}{1 + e^{\frac{A22 I_m}{In}}} \right]
 \end{aligned} \tag{2.1.1}$$

```

> # Insert data optimized using DE
data := [R00 = 0.0920607, R10 = 9.71807, R20 = 0.0506281,
C1 = 1.0,
Em0 = 12.623, KE = 0.623657,
A0 = 0.347071,
A21 = 3.62106,
A22 = 7.10553,
Cn = 4.54474,
Ac = 0.0077,
delta = 0.64741,
In = 1.90781,
#C(0,0) = 570,
#C(max(0, I__1), 0) = 570,
tau1 = 44499,
theta = 25,
theta__n = 25,
theta__f = 24,
epsilon = 1
]

```

```

data := [R00 = 0.0920607, R10 = 9.71807, R20 = 0.0506281, C1 = 1.0, Em0 = 12.623,
KE = 0.623657, A0 = 0.347071, A21 = 3.62106, A22 = 7.10553, Cn = 4.54474, Ac
= 0.0077, delta = 0.64741, In = 1.90781, tau1 = 44499, theta = 25, theta_n = 25, theta_f = 24, epsilon = 1]
\tag{2.1.2}

```

> subs(data,params)

$$\left[SOC = 1 - 0.001694266338 Q_e, DOC = 1 - 0.2200345894 Q_e (0.0077 \right. \quad (2.1.3)$$

$$\left. + 0.6531632611 \max(0, I_l)^{0.64741} \right), Em = -173.226786 + 185.849786 SOC, R0$$

$$= 0.1240122992 - 0.03195159921 SOC, R1 = -9.71807 \ln(DOC), R2$$

$$= \frac{0.0506281 e^{3.62106(1-SOC)}}{1 + e^{\frac{3.724443210 I_m}{m}}} \right]$$

Define the differential equations using the simplified model in the paper

> # Model simplified Equation

```
eqns := [Q__e = I__0*t,
          I__1 = I__0*(1-exp(-t/tau1)),
          V0 = Em - (R1*(1 - exp(-t/tau1)) + R0 + R2)*I__0
        ]
```

```
:
<%>
```

$$\left[\begin{array}{l} Q_e = I_0 t \\ I_l = I_0 \left(1 - e^{-\frac{t}{\tau_l}} \right) \\ V0 = Em - \left(R1 \left(1 - e^{-\frac{t}{\tau_l}} \right) + R0 + R2 \right) I_0 \end{array} \right] \quad (2.1.4)$$

> # Semplification done in the paper

$$I_m := \text{subs}(\text{data}, I_0); \quad I_m := I_0 \quad (2.1.5)$$

> soll := solve(subs(params,data,eqns), [Q__e, I__1, V0])

$$soll := \left[\left[Q_e = I_0 t, I_l = -1. I_0 e^{-0.00002247241511 t} + I_0, V0 = \right. \right. \quad (2.1.6)$$

$$\left. - \frac{1}{1. + e^{\frac{3.724443210 I_0}{m}}} \left(1.000000000 \times 10^{-11} \left(9.718070000 \right. \right. \right.$$

$$\left. \times 10^{11} I_0 e^{-0.00002247241511 t} \ln(DOC) e^{\frac{3.724443210 I_0}{m}} + 9.718070000 \right.$$

$$\left. \times 10^{11} I_0 e^{-0.00002247241511 t} \ln(DOC) - 9.718070000 \times 10^{11} I_0 \ln(DOC) e^{\frac{3.724443210 I_0}{m}} \right]$$

$$\begin{aligned}
& - 3.195159921 \times 10^9 I_0 e^{3.724443210 I_0} SOC - 9.718070000 \times 10^{11} I_0 \ln(DOC) \\
& + 5.062810000 \times 10^9 I_0 e^{3.62106(1-SOC)} + 1.240122992 \times 10^{10} I_0 e^{3.724443210 I_0} \\
& - 3.195159921 \times 10^9 I_0 SOC - 1.858497860 \times 10^{13} SOC e^{3.724443210 I_0} \\
& + 1.240122992 \times 10^{10} I_0 + 1.732267860 \times 10^{13} e^{3.724443210 I_0} - 1.858497860 \\
& \times 10^{13} SOC + 1.732267860 \times 10^{13} \Big) \Big) \Big]
\end{aligned}$$

> eqns_battery := subs(sol1[1,1], sol1[1,2], data, params)

$$eqns_{battery} := \left[SOC = 1 - 0.001694266338 I_0 t, DOC = 1 - 0.2200345894 I_0 t \left(0.0077 \right. \right. \quad (2.1.7)$$

$$+ 0.6531632611 \max(0, -1. I_0 e^{-0.00002247241511 t} + I_0)^{0.64741} \Big), Em = -173.226786$$

$$+ 185.849786 SOC, R0 = 0.1240122992 - 0.03195159921 SOC, RI =$$

$$-9.71807 \ln(DOC), R2 = \frac{0.0506281 e^{3.62106(1-SOC)}}{1 + e^{3.724443210 I_0}} \Big]$$

> simplify(subs(%, sol1[1,3]))

$$\begin{aligned}
V0 = & \frac{1}{1000.000000 + 1000.000000 e^{3.72444321 I_0}} \Big(12623. + I_0 \Big(\\
& -9718.07 e^{-0.00002247241511 t + 3.72444321 I_0} - 9718.07 e^{-0.00002247241511 t} \\
& + 9718.07 e^{3.72444321 I_0} + 9718.07 \Big) \ln(1 - 0.001694266338 I_0 t \\
& - 0.1437185100 I_0 t \max(0, I_0 (1. - 1. e^{-0.00002247241511 t}))^{0.64741} \Big) + (12623. \\
& - 0.05413451899 I_0^2 t + (-92.06069999 - 314.8790363 t) I_0) e^{3.72444321 I_0} \\
& - 0.05413451899 I_0^2 t + (-1984.39563 - 314.8790363 t) I_0 \Big)
\end{aligned} \quad (2.1.8)$$

Equation of the Voltage of the Battery (discharge)

> V0plot := simplify(evalf(op(2,%)))

$$\begin{aligned}
V0plot := & \frac{1}{1000.000000 + 1000.000000 e^{3.72444321 I_0}} \Big(12623. + I_0 \Big(\\
& -9718.07 e^{-0.00002247241511 t + 3.72444321 I_0} - 9718.07 e^{-0.00002247241511 t}
\end{aligned} \quad (2.1.9)$$

$$\begin{aligned}
& + 9718.07 e^{3.72444321 I_0 t} + 9718.07 \ln(1 - 0.001694266338 I_0 t \\
& - 0.1437185100 I_0 t \max(0, I_0 (1 - 1 \cdot e^{-0.00002247241511 t}))^{0.64741}) + (12623. \\
& - 0.05413451899 I_0^2 t + (-92.06069999 - 314.8790363 t) I_0) e^{3.72444321 I_0 t} \\
& - 0.05413451899 I_0^2 t + (-1984.39563 - 314.8790363 t) I_0)
\end{aligned}$$

Define V0 as a function of time and current

```
> V0__func := simplify(unapply(V0plot, t, I__0));
```


$$\begin{aligned}
V0_{func} := (t, I_0) \mapsto & \frac{1}{1000.000000 + 1000.000000 \cdot e^{3.72444321 \cdot I_0 t} - 9718.07 \cdot e^{-0.00002247241511 \cdot t + 3.72444321 \cdot I_0 t} - 9718.07 \cdot e^{-0.00002247241511 \cdot t} + 9718.07} \\
& \cdot e^{3.72444321 \cdot I_0 t} + 9718.07) \cdot \ln(1 - 0.001694266338 \cdot I_0 \cdot t - 0.1437185100 \cdot I_0 \cdot t \\
& \cdot \max(0, I_0 \cdot (1 - 1 \cdot e^{-0.00002247241511 \cdot t}))^{0.64741}) + (12623. - 0.05413451899 \cdot I_0^2 \cdot t \\
& + (-92.06069999 - 314.8790363 \cdot t) \cdot I_0) \cdot e^{3.72444321 \cdot I_0 t} - 0.05413451899 \cdot I_0^2 \cdot t \\
& + (-1984.39563 - 314.8790363 \cdot t) \cdot I_0)
\end{aligned} \tag{2.1.10}$$

Plot the discharge of the battery like in the paper "Hybrid vehicle optimization: lead acid battery modellization"

```
> display(semilogplot(V0__func(t,12), t=10^(-1)..0.9,color=
violet, legend = "12 A"),

          semilogplot(V0__func(t,8), t=10^(-1)..1.4,color =
purple, legend = "8 A"),
          semilogplot(V0__func(t,4), t=10^(-1)..3,color = blue,
legend = "4 A"),
          semilogplot(V0__func(t,2.4), t=10^(-1)..5,color = green,
legend = "2.4 A"),
          semilogplot(V0__func(t,1.6), t=10^(-1)..8,color = yellow,
legend = "1.6 A"),
          semilogplot(V0__func(t,0.8), t=10^(-1)..16,color =
orange, legend = "0.8 A"),
          semilogplot(V0__func(t,0.4), t=10^(-1)..28,color = red, legend
= "0.4 A"),
          labels = ["Time-log (min)", V__0],
          view = [10^(-1)..100, 0..13],
          size = [1000, 500])
```

);

 


The discharge plot obtained are comparable with the curve shown in the paper: "Hybrid vehicle optimization: lead acid battery modellization"

Define the equation of the State of Charge of the battery

```
> SOC1 := unapply(rhs(subs(data,params,eqns__battery[1])), [t, I_0]);
```

$$SOC1 := (t, I_0) \mapsto 1 - 0.001694266338 \cdot I_0 \cdot t \quad (2.1.11)$$
 
```
> display(plot(SOC1(t,5),t=10^(-1)..7.5));
```



Charging the battery

Define the parameters in order to simulate the charge of the battery

```
> # Parameters
```

```
params2 := [
  SOCc = 0.94 + Q__e/Capacity(0,theta), # The value 0.94 of
  SOC it used to define the battery completly discharged
  DOCc = 0.94 + Q__e/Capacity(I__1,theta),
  E__mc = Em0-KE*(273+theta)*(1-SOCc),

  R__0c = R00*(1 + A0*(1 - SOCc)),
  R__1c = -R10*log(DOCc),
  R__2c = R20*( exp(A21(1 - SOCc))/( 1 + exp (A22*I__m/In)))
];
```

$$\begin{aligned}
 \text{params2} := & \left[\text{SOCc} = 0.94 + \frac{Q_e Ac}{Cn \left(\frac{\theta - \theta_f}{\theta_n - \theta_f} \right)^\epsilon}, \text{DOCc} = 0.94 \right. \\
 & + \frac{Q_e \left(Ac + (1 - Ac) \left(\frac{\max(0, I_l)}{I_n} \right)^\delta \right)}{Cn \left(\frac{\theta - \theta_f}{\theta_n - \theta_f} \right)^\epsilon}, E_{mc} = Em0 - KE (273 + \theta) (1 \\
 & \left. - \text{SOCc}), R_{0c} = R00 (1 + A0 (1 - \text{SOCc})), R_{1c} = -R10 \ln(\text{DOCc}), R_{2c} \right. \\
 & \left. - \text{SOCc} \right]
 \end{aligned} \tag{2.1.1.1}$$

$$= \frac{R_{20} e^{A_{21}(1-SOC_c)}}{1 + e^{\frac{A_{22} I_0}{I_n}}}$$

> subs(data,params2)

$$SOC_c = 0.94 + 0.001694266338 Q_e, DOC_c = 0.94 + 0.2200345894 Q_e (0.0077 \quad (2.1.1.2)$$

$$+ 0.6531632611 \max(0, I_l)^{0.64741}, E_{mc} = -173.226786$$

$$+ 185.849786 SOC_c, R_{0c} = 0.1240122992 - 0.03195159921 SOC_c, R_{lc} =$$

$$-9.71807 \ln(DOC_c), R_{2c} = \frac{0.0506281 e^{3.62106(1-SOC_c)}}{1 + e^{\frac{3.724443210 I_0}{I_n}}}$$

Define the differential equations using the given simplified model

> # Model simplified Equation

```
eqns__2 := [Q__e = I__0*t,
             I__1 = I__0*(1-exp(-t/tau1)),
             V0 = E__mc - (R__lc*(1 - exp(-t/tau1)) + R__0c +
             R__2c)*I__0
             ]
:
<%>
```

$$\begin{bmatrix} Q_e = I_0 t \\ I_l = I_0 \left(1 - e^{-\frac{t}{\tau_l}}\right) \\ V0 = E_{mc} - \left(R_{lc} \left(1 - e^{-\frac{t}{\tau_l}}\right) + R_{0c} + R_{2c}\right) I_0 \end{bmatrix} \quad (2.1.1.3)$$

> solc := solve(subs(params2,data,eqns__2),[Q__e,I__1,V0])

$$solc := \left[\begin{bmatrix} Q_e = I_0 t, I_l = -1. I_0 e^{-0.00002247241511 t} + I_0, V0 = \end{bmatrix} \quad (2.1.1.4)$$

$$- \frac{1}{1. + e^{\frac{3.724443210 I_0}{I_n}}} \left(1.0000000000 \times 10^{-11} \left(9.718070000 \right.$$

$$\times 10^{11} I_0 e^{-0.00002247241511 t} \ln(DOC_c) e^{\frac{3.724443210 I_0}{I_n}} + 9.718070000$$

$$\times 10^{11} I_0 e^{-0.00002247241511 t} \ln(DOC_c) - 9.718070000$$

$$\begin{aligned}
& \times 10^{11} I_0 \ln(DOCc) e^{3.724443210 I_0} - 3.195159921 \times 10^9 I_0 e^{3.724443210 I_0} SOCc \\
& - 9.718070000 \times 10^{11} I_0 \ln(DOCc) + 5.062810000 \times 10^9 I_0 e^{3.62106(1-SOCc)} \\
& + 1.240122992 \times 10^{10} I_0 e^{3.724443210 I_0} - 3.195159921 \times 10^9 I_0 SOCc \\
& - 1.858497860 \times 10^{13} SOCc e^{3.724443210 I_0} + 1.240122992 \times 10^{10} I_0 \\
& + 1.732267860 \times 10^{13} e^{3.724443210 I_0} - 1.858497860 \times 10^{13} SOCc \\
& + 1.732267860 \times 10^{13} \Big) \Big) \Big) \Big]
\end{aligned}$$

> eqns__battery2 := subs(solc[1,1],solc[1,2],data,params2)

$$eqns_{battery2} := \left[SOCc = 0.94 + 0.001694266338 I_0 t, DOCc = 0.94 \right] \quad (2.1.1.5)$$

$$+ 0.2200345894 I_0 t \left(0.0077 + 0.6531632611 \max(0,$$

$$- 1. I_0 e^{-0.00002247241511 t} + I_0 \Big)^{0.64741} \Big), E_{mc} = -173.226786$$

$$+ 185.849786 SOCc, R_{oc} = 0.1240122992 - 0.03195159921 SOCc, R_{lc} =$$

$$- 9.71807 \ln(DOCc), R_{2c} = \frac{0.0506281 e^{3.62106(1-SOCc)}}{1 + e^{3.724443210 I_0}} \Big]$$

> simplify(subs(eqns__battery2,solc[1,3]))

$$V0 = \frac{1}{1. + e^{3.72444321 I_0}} \left(1.4720128 + I_0 \left(-9.71807 e^{-0.00002247241511 t + 3.72444321 I_0} \right) \right) \quad (2.1.1.6)$$

$$- 9.71807 e^{-0.00002247241511 t} + 9.71807 e^{3.72444321 I_0} + 9.71807 \Big) \ln(0.94$$

$$+ 0.001694266338 I_0 t + 0.1437185100 I_0 t \max(0, I_0 (1.$$

$$- 1. e^{-0.00002247241511 t} \Big)^{0.64741} \Big) + (1.4720128 + 0.00005413451899 I_0^2 t + ($$

$$- 0.09397779594 + 0.3148790363 t) I_0 \Big) e^{3.72444321 I_0} + 0.00005413451899 I_0^2 t$$

$$+ (-1.986312726 + 0.3148790363 t) I_0 \Big)$$

Equation of the Voltage of the Battery (charge)

> V0plotc := simplify(evalf(op(2,%)))

(2.1.1.7)

$$V0plotc := \frac{1}{1. + e^{-0.00002247241511 \cdot t + 3.72444321 \cdot I_0}} \left(1.4720128 + I_0 \cdot \left(-9.71807 \cdot e^{-0.00002247241511 \cdot t + 3.72444321 \cdot I_0} - 9.71807 \cdot e^{-0.00002247241511 \cdot t} + 9.71807 \cdot e^{3.72444321 \cdot I_0} + 9.71807 \right) \ln(0.94 + 0.001694266338 \cdot I_0 \cdot t + 0.1437185100 \cdot I_0 \cdot t \max(0., I_0 (1. - 1. \cdot e^{-0.00002247241511 \cdot t}))^{0.64741}) + (1.4720128 + 0.00005413451899 \cdot I_0^2 \cdot t + (-0.09397779594 + 0.3148790363 \cdot t) \cdot I_0) \cdot e^{3.72444321 \cdot I_0} + 0.00005413451899 \cdot I_0^2 \cdot t + (-1.986312726 + 0.3148790363 \cdot t) \cdot I_0 \right) \quad (2.1.1.7)$$

Define V0 as a function of time and current

```
> V0__funcc := simplify(unapply(V0plotc, t, I__0));
```


$$V0_{funcc} := (t, I_0) \mapsto \frac{1}{1. + e^{-0.00002247241511 \cdot t + 3.72444321 \cdot I_0}} \left(1.4720128 + I_0 \cdot \left(-9.71807 \cdot e^{-0.00002247241511 \cdot t + 3.72444321 \cdot I_0} - 9.71807 \cdot e^{-0.00002247241511 \cdot t} + 9.71807 \cdot e^{3.72444321 \cdot I_0} + 9.71807 \right) \cdot \ln(0.94 + 0.001694266338 \cdot I_0 \cdot t + 0.1437185100 \cdot I_0 \cdot t \max(0., I_0 (1. - 1. \cdot e^{-0.00002247241511 \cdot t}))^{0.64741}) + (1.4720128 + 0.00005413451899 \cdot I_0^2 \cdot t + (-0.09397779594 + 0.3148790363 \cdot t) \cdot I_0) \cdot e^{3.72444321 \cdot I_0} + 0.00005413451899 \cdot I_0^2 \cdot t + (-1.986312726 + 0.3148790363 \cdot t) \cdot I_0 \right) \quad (2.1.1.8)$$

Plot the charge of the battery with different values of current I0

```
> display(semilogplot(V0__funcc(t,12), t=10^(-1)..3.5,color=
violet, legend = "12 A"),

          semilogplot(V0__funcc(t,8), t=10^(-1)..5.2,color =
purple, legend = "8 A"),
          semilogplot(V0__funcc(t,4), t=10^(-1)..10,color =
blue, legend = "4 A"),
          semilogplot(V0__funcc(t,2.4), t=10^(-1)..17,color = green,
legend = "2.4 A"),
          semilogplot(V0__funcc(t,1.6), t=10^(-1)..25,color = yellow,
legend = "1.6 A"),
          semilogplot(V0__funcc(t,0.8), t=10^(-1)..50,color =
orange, legend = "0.8 A"),
```

 
```
semilogplot(V0__funcc(t,0.4), t=10^(-1)..100,color = red,
legend = "0.4 A"),
labels = ["Time-log (min)", V__0charge],
view = [10^(-1)..100, 0..13],
size = [1000, 500]
);
```




▼ PV Panel Model

▼ Solar Cell equivalent model: single diode

Single Diode Model

 

Linear Graph - DDM

 

The diode equation writes :

$$I_d = I_s \left(e^{\frac{V_d}{\eta V_{th}}} - 1 \right)$$

where $V_{th} = \frac{k_B T}{q}$ is the thermal voltage.

> eq_Vth := V__th = k__B*T/q

$$eq_Vth := V_{th} = \frac{k_B T}{q} \quad (3.1.1)$$

> data := k__B=1.38062*10^(-23), T =300, q =1.60219*10^(-19),
I__ds = 1.2172e-9, Rs = 9.2/1000, Rh =12.7, eta = 1.13:
subs(%,eq_Vth);


data_full := %, %%;

I__d = I__ds*(exp(V__d/(eta*V__th)) - 1);

plot(subs(%%,data_full,eta=1,rhs(%%)), V__d = 0..0.75);
 $V_{th} = 0.02585124111$

data_full := $V_{th} = 0.02585124111, k_B = 1.380620000 \times 10^{-23}, T = 300, q = 1.602190000$
 $\times 10^{-19}, I_{ds} = 1.2172 \times 10^{-9}, R_s = 0.009200000000, R_h = 12.7, \eta = 1.13$
 
$$I_d = I_{ds} \left(e^{\frac{V_d}{\eta V_{th}}} - 1 \right)$$



Linear Graph of the electrical system

List of **vertices** (or nodes)

```
> V := [a,b,g];
```

$$V := [a, b, g] \quad (3.2.1)$$

The list of **edges** (correspond to physical elements) and we must also specify the .

The order is defined according to the arrow in the second picture.

```
> E := [[a,g], # element Eph
        [g,a], # element D1: diode 1
        [g,a], # element Rh: shunt resistance
        [a,b], # element Rs: series resistance
        [g,b] # element V: output
        ];
```

$$E := [[a, g], [g, a], [g, a], [a, b], [g, b]] \quad (3.2.2)$$

Through and across variables

Through variables (current)

```
> tau_vars := [i_ph(t), i_d(t), i_Rh(t), i_Rs(t), i_pv(t)];
```

$$\tau_{vars} := [i_{ph}(t), i_d(t), i_{Rh}(t), i_{Rs}(t), i_{pv}(t)] \quad (3.2.3)$$

Across variables (voltages)

```
> alpha_vars := [v_ph(t), v_d(t), v_Rh(t), v_Rs(t), v_pv(t)];
```

$$\alpha_{vars} := [v_{ph}(t), v_d(t), v_{Rh}(t), v_{Rs}(t), v_{pv}(t)] \quad (3.2.4)$$

Create a procedure to get the incidence matrix providing the list of nodes and the list of edges

```
> build_incidence_matrix := proc(V::list,E::list(list),$)
```

```

local im, i, j, v, e;

# create empty incidence matrix
im := Matrix(1..nops(V),1..nops(E),fill=0):

for j from 1 to nops(V) do
  v := V[j]; # j-th node

  # loop over the edges and check if the node is in
  for i from 1 to nops(E) do
    #print(type(E[i],list);
    #if nops(E[i]) > 1 then
    # e := E[i][1]; # i-th edge
    #else
    e := E[i]; # i-th edge
    #end ;
    #print(e,v=e[1]);
    if has(e,v) and (v = e[1] ) then # check v is in e and
v is first element in e
      im[j,i] := +1;
    elif has(e,v) and (v = e[2] ) then # check v is in e
and v is second element in e
      im[j,i] := -1;
    else
      im[j,i] := 0; # v is not in e
    end;
  end do:
end do:

return im;

end proc:

```

Incidence matrix

```

> IM0 := build_incidence_matrix(V,E);
DF := DataFrame(IM0, columns = [seq(e__||i,i=1..nops(E))],
               rows      = convert(V,list),
               datatypes=[seq(integer,i=1..nops(E))]);

```

$$IM0 := \begin{bmatrix} 1 & -1 & -1 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 \\ -1 & 1 & 1 & 0 & 1 \end{bmatrix}$$

$$DF := \begin{bmatrix} & e_1 & e_2 & e_3 & e_4 & e_5 \\ a & 1 & -1 & -1 & 1 & 0 \\ b & 0 & 0 & 0 & -1 & -1 \\ g & -1 & 1 & 1 & 0 & 1 \end{bmatrix} \quad (3.2.5)$$

As expected is singular

> GaussianElimination(IM0)

$$\begin{bmatrix} 1 & -1 & -1 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \quad (3.2.6)$$

I remove the ground node and get a linearly independent set of rows

> A_mat := IM0[1..-2,1..-1];

$$A_mat := \begin{bmatrix} 1 & -1 & -1 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 \end{bmatrix} \quad (3.2.7)$$

Compute the number of nodes, vertices, branches and chords

```
> nv := nops(V);
nb := nv-1;
ne := nops(E);
nc := ne-nb;
```

nv := 3

nb := 2

ne := 5

nc := 3

(3.2.8)

Reduce in the echelon form and extract Ib and Ac matrices

```
> Af_mat := ReducedRowEchelonForm(A_mat);
Ib_mat := Af_mat[1..nb,1..nb];
Ac_mat := Af_mat[1..nb,nb+1..-1];
```

nc := *ne*-*nb*;

$$Af_mat := \begin{bmatrix} 1 & -1 & -1 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix}$$

$$Ib_mat := \begin{bmatrix} 1 & -1 \\ 0 & 0 \end{bmatrix}$$

$$Ac_mat := \begin{bmatrix} -1 & 0 & -1 \\ 0 & 1 & 1 \end{bmatrix}$$

$$nc := 3$$

(3.2.9)

Matrix Bf is the **circuit matrix** that contains the set of fundamental circuits or loops (i.e. independent circuits)

```
> NullSpace(Af_mat); # find the orthogonal
tmp_Bf := Transpose(Matrix([op(%)]));
```

$$\left\{ \begin{bmatrix} 1 \\ 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}, \begin{bmatrix} 1 \\ 1 \\ 0 \\ 0 \\ 0 \end{bmatrix}, \begin{bmatrix} 1 \\ 0 \\ 0 \\ -1 \\ 1 \end{bmatrix} \right\}$$

$$tmp_Bf := \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & -1 & 1 \end{bmatrix} \quad (3.2.10)$$

Proof that they are orthogonal

It represents a general conservation principle, applicable to any type of physical system represented by a linear graph.

This Principle of Orthogonality can be used to derive Tellegen's Theorem or the Principle of Virtual Work for mechanical systems.

```
> Af_mat.Transpose(tmp_Bf);
```

$$\begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \quad (3.2.11)$$

We can get the matrix also

```
Af_mat = <lb_mat | Ac_mat>;
```

```
Bf_mat = <Bb_mat | Ic_mat>;
```

```
Af_mat.Bf_mat^T = 0 --> <lb_mat | Ac_mat><Bb_mat |
Ic_mat>^T = 0 --> lb_mat.Bb_mat^T = -Ac_mat.Ic_mat^T
--> Bb_mat^T = -Ac_mat --> Bb_mat = -Ac_mat^T
```

```
> Ic_mat := IdentityMatrix(nc):
```

```
Bb_mat := -Transpose(Ac_mat):
```

```
Bf_mat := <Bb_mat | Ic_mat>:
```

```
Ic_mat, Bb_mat, Bf_mat ;
```

```
#check that it is correct
```

```
Bf_mat = tmp_Bf;
```

```
Bf_mat := tmp_Bf;
```

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}, \begin{bmatrix} 1 & 0 \\ 0 & -1 \\ 1 & -1 \end{bmatrix}, \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 \\ 1 & -1 & 0 & 0 & 1 \end{bmatrix} \\
 \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 \\ 1 & -1 & 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & -1 & 1 \end{bmatrix} \\
 Bf_mat := \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & -1 & 1 \end{bmatrix} \quad (3.2.12)$$

Cutset or node equations

Obtain the cutset equations

```
> cutset_eqns := Af_mat.<tau_vars>;
```

```
#latex(cutset_eqns)
```

$$cutset_eqns := \begin{bmatrix} i_{ph}(t) - i_d(t) - i_{Rh}(t) - i_{pv}(t) \\ i_{Rs}(t) + i_{pv}(t) \end{bmatrix} \quad (3.2.13)$$

We can also exploit the echelon form to solve the branch through variables as function of chords through variables

```
> Ib_mat.<tau_vars[1..nb]> = -Ac_mat.<tau_vars[nb+1..-1]>;
```

```
#sol_tau_b := op(solve(cutset_eqns,tau_vars[1..nb])): #
```

```
verificare
```

```
sol_tau_b := op(solve(cutset_eqns,[i_ph(t),i_Rs(t)])):
```

```
<sol_tau_b>
```

$$\begin{bmatrix} i_{ph}(t) - i_d(t) \\ 0 \end{bmatrix} = \begin{bmatrix} i_{Rh}(t) + i_{pv}(t) \\ -i_{Rs}(t) - i_{pv}(t) \end{bmatrix} \\
 \begin{bmatrix} i_{ph}(t) = i_d(t) + i_{Rh}(t) + i_{pv}(t) \\ i_{Rs}(t) = -i_{pv}(t) \end{bmatrix} \quad (3.2.14)$$

```
> tau_vars[1..nb];
```

$$[i_{ph}(t), i_d(t)] \quad (3.2.15)$$

```
> Ib_mat;
```

$$(3.2.16)$$

$$\begin{bmatrix} 1 & -1 \\ 0 & 0 \end{bmatrix} \quad (3.2.16)$$

```
> <tau_vars[1..nb]>;
```

$$\begin{bmatrix} i_{ph}(t) \\ i_d(t) \end{bmatrix} \quad (3.2.17)$$

```
> Ib_mat.<tau_vars[1..nb]> = -Ac_mat.<tau_vars[nb+1..-1]>;
```

$$\begin{bmatrix} i_{ph}(t) - i_d(t) \\ 0 \end{bmatrix} = \begin{bmatrix} i_{Rh}(t) + i_{pv}(t) \\ -i_{Rs}(t) - i_{pv}(t) \end{bmatrix} \quad (3.2.18)$$

Circuit equations

Circuit or loop equations

```
> circuit_eqns := Bf_mat.<alpha_vars>;
```

```
#latex(circuit_eqns)
```

$$circuit_eqns := \begin{bmatrix} v_{ph}(t) + v_{Rh}(t) \\ v_{ph}(t) + v_d(t) \\ v_{ph}(t) - v_{Rs}(t) + v_{pv}(t) \end{bmatrix} \quad (3.2.19)$$

We can also solve the chords across variables as function of the branch across variables

```
> sol_alpha_c := op(solve(circuit_eqns,alpha_vars[1..nc])):
<sol_alpha_c>;
```

$$\begin{bmatrix} v_{ph}(t) = v_{Rs}(t) - v_{pv}(t) \\ v_d(t) = -v_{Rs}(t) + v_{pv}(t) \\ v_{Rh}(t) = -v_{Rs}(t) + v_{pv}(t) \end{bmatrix} \quad (3.2.20)$$

Constitutive equations of each physical element

Elements constitutive (or terminal) equations

```
> const_elem_eqns :=
  <i__ph(t) = i__ph_law(t),
  i__d(t) = I__ds*(exp(v__d(t)/(eta*V__th)) - 1),
  v__Rs(t) = Rs*i__Rs(t),
  v__Rh(t) = Rh*i__Rh(t),
```

```
v__pv(t) = v__pv__law(t)
>: <%>
```

$$\begin{bmatrix} i_{ph}(t) = i_{ph_{law}}(t) \\ i_d(t) = I_{ds} \left(e^{\frac{v_d(t)}{\eta V_{th}}} - 1 \right) \\ v_{Rs}(t) = R_s i_{Rs}(t) \\ v_{Rh}(t) = R_h i_{Rh}(t) \\ v_{pv}(t) = v_{pv_{law}}(t) \end{bmatrix} \quad (3.2.21)$$

```
> i__s1(t),i__s2(t); # can be constnat or function of time (in
this case via temperatures)
i__s1(t), i__s2(t) \quad (3.2.22)
```

```
> circuit_eqns;
cutset_eqns;
```

$$\begin{bmatrix} v_{ph}(t) + v_{Rh}(t) \\ v_{ph}(t) + v_d(t) \\ v_{ph}(t) - v_{Rs}(t) + v_{pv}(t) \end{bmatrix} \quad \begin{bmatrix} i_{ph}(t) - i_d(t) - i_{Rh}(t) - i_{pv}(t) \\ i_{Rs}(t) + i_{pv}(t) \end{bmatrix} \quad (3.2.23)$$

```
> #latex(const_elem_eqns)
```

```
List of equations of photovoltaic cell
```

```
> pvc_eqns := <const_elem_eqns,circuit_eqns,cutset_eqns>
```

(3.2.24)

$$pvc_eqns := \left[\begin{array}{l} i_{ph}(t) = i_{phlaw}(t) \\ i_d(t) = I_{ds} \left(e^{\frac{v_d(t)}{\eta V_{th}}} - 1 \right) \\ v_{Rs}(t) = R_S i_{Rs}(t) \\ v_{Rh}(t) = R_h i_{Rh}(t) \\ v_{pv}(t) = v_{pvlaw}(t) \\ v_{ph}(t) + v_{Rh}(t) \\ v_{ph}(t) + v_d(t) \\ v_{ph}(t) - v_{Rs}(t) + v_{pv}(t) \\ i_{ph}(t) - i_d(t) - i_{Rh}(t) - i_{pv}(t) \\ i_{Rs}(t) + i_{pv}(t) \end{array} \right] \quad (3.2.24)$$

Analytical solution of equivalent circuit of a photovoltaic cell

```
> pvc_vars := [op(tau_vars), op(alpha_vars)];
pvc_vars := [i_ph(t), i_d(t), i_Rh(t), i_Rs(t), i_pv(t), v_ph(t), v_d(t), v_Rh(t), v_Rs(t), v_pv(t)] (3.2.25)
```

Check that variables are equal in number to the equations

```
> RowDimension(pvc_eqns) = nops(tau_vars)+nops(alpha_vars) ;
10 = 10 (3.2.26)
```

```
> sol_pvc := fullsimplify(solve(convert(pvc_eqns, set), convert
(pvc_vars, set))):
<op(%)>:
```

Partial solution of the equations of the equivalent circuit to show the relationship of

```
> convert(convert(pvc_eqns, list)[1..-3], set) union convert
(pvc_eqns[-1], set);
convert(pvc_vars, set) minus {i__pv(t)};

solve(%%, %);
SDM_pv_eqn := collect(subs(%, pvc_eqns[-2]), I__ds);
```

$$\left\{ \begin{array}{l} i_{Rs}(t) + i_{pv}(t), v_{ph}(t) + v_{Rh}(t), v_{ph}(t) + v_d(t), v_{ph}(t) - v_{Rs}(t) + v_{pv}(t), i_d(t) \end{array} \right.$$

$$\begin{aligned}
&= I_{ds} \left(e^{\frac{v_d(t)}{\eta V_{th}}} - 1 \right), i_{ph}(t) = i_{ph_{law}}(t), v_{Rh}(t) = Rh i_{Rh}(t), v_{Rs}(t) = Rs i_{Rs}(t), v_{pv}(t) \\
&= v_{pv_{law}}(t) \left\{ \begin{aligned} &\{i_{Rh}(t), i_{Rs}(t), i_d(t), i_{ph}(t), v_{Rh}(t), v_{Rs}(t), v_d(t), v_{ph}(t), v_{pv}(t)\} \\ &\left\{ \begin{aligned} &i_{Rh}(t) = \frac{Rs i_{pv}(t) + v_{pv_{law}}(t)}{Rh}, i_{Rs}(t) = -i_{pv}(t), i_d(t) = I_{ds} e^{\frac{Rs i_{pv}(t) + v_{pv_{law}}(t)}{\eta V_{th}}} - I_{ds}, \\ &i_{ph}(t) = i_{ph_{law}}(t), v_{Rh}(t) = Rs i_{pv}(t) + v_{pv_{law}}(t), v_{Rs}(t) = -Rs i_{pv}(t), v_d(t) = Rs i_{pv}(t) \\ &+ v_{pv_{law}}(t), v_{ph}(t) = -Rs i_{pv}(t) - v_{pv_{law}}(t), v_{pv}(t) = v_{pv_{law}}(t) \end{aligned} \right\} \end{aligned} \right. \\
&SDM_{pv_eqn} := \quad \quad \quad (3.2.27) \\
&\left[\begin{aligned} &\left(\frac{Rs i_{pv}(t) + v_{pv_{law}}(t)}{\eta V_{th}} + 1 \right) I_{ds} + i_{ph_{law}}(t) - \frac{Rs i_{pv}(t) + v_{pv_{law}}(t)}{Rh} \dots \end{aligned} \right]
\end{aligned}$$

Output current of the cell

The pannel output current i_{pv} in term of the output voltage v_{pv} :

```
> simplify(solve(SDM_pv_eqn,{i__pv(t)}));
tmp := rhs(%[1]);
```

```
Iout := unapply(subs(i__ph__law(t) = I__ph, v__pv__law(t)=
V__pv, tmp) ,[V__pv]);
```

$$\begin{aligned}
&\left\{ \begin{aligned} &i_{pv}(t) = \frac{1}{(Rh + Rs) Rs} \left(- (Rh \right. \\ &\left. + Rs) \eta V_{th} \text{LambertW} \left(\frac{\left(\frac{I_{ds} Rs + i_{ph_{law}}(t) Rs + v_{pv_{law}}(t)}{(Rh + Rs) \eta V_{th}} \right) Rh}{(Rh + Rs) \eta V_{th}} \right) + Rs \left(I_{ds} Rh \right. \\ &\left. \left. + i_{ph_{law}}(t) Rh - v_{pv_{law}}(t) \right) \right) \end{aligned} \right\}
\end{aligned}$$

$$\begin{aligned}
tmp &:= \frac{1}{(Rh + Rs) Rs} \left(- (Rh \right. \\
&\quad \left. + Rs) \eta V_{th} \text{LambertW} \left(\frac{\left(\frac{I_{ds} Rs + i_{ph_{law}}(t) Rs + v_{pv_{law}}(t)}{(Rh + Rs) \eta V_{th}} \right) Rh}{I_{ds} Rs Rh e} \right) + Rs \left(I_{ds} Rh \right. \\
&\quad \left. + i_{ph_{law}}(t) Rh - v_{pv_{law}}(t) \right) \left. \right) \\
I_{out} &:= V_{pv} \mapsto \frac{1}{(Rh + Rs) \cdot Rs} \left(- (Rh + Rs) \cdot \eta \cdot V_{th} \right. \\
&\quad \left. \cdot \text{LambertW} \left(\frac{\left(\frac{I_{ds} \cdot Rs + I_{ph} \cdot Rs + V_{pv}}{(Rh + Rs) \cdot \eta \cdot V_{th}} \right) \cdot Rh}{I_{ds} \cdot Rs \cdot Rh \cdot e} \right) + Rs \cdot \left(I_{ds} \cdot Rh + I_{ph} \cdot Rh - V_{pv} \right) \right)
\end{aligned} \tag{3.2.28}$$

Output voltage of the cell

We can also solve equation and give the expression of the output voltage V_{out} in term of the output current I_{out} :

```
> simplify(solve(SDM_pv_eqn,{v__pv__law(t)}));
tmp := rhs(%[1]);
```

```
Vout := unapply(subs(i__ph__law(t) = I__ph, i__pv(t)= I__pv,
v__pv__law(t)= V__pv, tmp) ,[I__pv]);
```

$$\left\{ \begin{aligned}
v_{pv_{law}}(t) &= -\text{LambertW} \left(\frac{I_{ds} Rh e}{\eta V_{th}} \right) \eta V_{th} + (-Rh - Rs) i_{pv}(t) \\
&\quad + (I_{ds} + i_{ph_{law}}(t)) Rh
\end{aligned} \right\}$$

$$\begin{aligned}
 tmp &:= -\text{LambertW} \left(\frac{I_{ds} Rh e^{\frac{Rh (I_{ds} - i_{pv}(t) + i_{ph_{law}}(t))}{\eta V_{th}}}}{\eta V_{th}} \right) \eta V_{th} + (-Rh - Rs) i_{pv}(t) \\
 &\quad + (I_{ds} + i_{ph_{law}}(t)) Rh \\
 V_{out} &:= I_{pv} \mapsto -\text{LambertW} \left(\frac{I_{ds} \cdot Rh \cdot e^{\frac{Rh \cdot (I_{ds} - I_{pv} + I_{ph})}{\eta \cdot V_{th}}}}{\eta \cdot V_{th}} \right) \cdot \eta \cdot V_{th} + (-Rh - Rs) \cdot I_{pv} \\
 &\quad + (I_{ds} + I_{ph}) \cdot Rh
 \end{aligned} \tag{3.2.29}$$

Short-circuit current I_{sc}

The analytical expression of the short-circuit current I_{sc} is obtained by setting $V_{out} = 0$ which corresponds to $R_{load} = 0$:

> Isc:=Iout(0);
 $I_{sc} :=$ (3.2.30)

$$\begin{aligned}
 &\frac{1}{(Rh + Rs) Rs} \left(- (Rh + Rs) \eta V_{th} \text{LambertW} \left(\frac{\left(\frac{I_{ds} Rs + I_{ph} Rs}{(Rh + Rs) \eta V_{th}} \right) Rh}{(Rh + Rs) \eta V_{th}} \right) \right. \\
 &\quad \left. + Rs (I_{ds} Rh + I_{ph} Rh) \right)
 \end{aligned}$$

Open-circuit voltage V_{oc}

The analytical expression of the open-circuit voltage V_{oc} is obtained by setting $I_{out} = 0$ which corresponds to $R_{load} = \infty$:

> Voc := Vout(0);

$$V_{oc} := -\text{LambertW} \left(\frac{I_{ds} Rh e^{\frac{Rh (I_{ds} + I_{ph})}{\eta V_{th}}}}{\eta V_{th}} \right) \eta V_{th} + (I_{ds} + I_{ph}) Rh \tag{3.2.31}$$

Numerical example

Solar induced current:

> i_ph = I_ph0*I_r/I_r0;

Ir is the irradiance (light intensity), in W/m2, falling on

the cell.

I_{ph0} is the measured solar-generated current for the irradiance I_{r0}.

$$i_{ph} = \frac{I_{ph0} I_r}{I_{r0}} \quad (3.3.1)$$

The previous equation will be used in the next section to model the solar current

```
> data_Ns := k_B=1.38062*10^(-23), T =300, q =1.60219*10^(-19),
```

```
    I_ds = Np*1.2172e-9,
```

```
    Rs = 9.2/1000*(Ns/Np), Rh =12.7*(Ns/Np), eta = 1.13;
```

```
    subs(%,lhs(eq_Vth) = rhs(eq_Vth)*Ns );
```

```
data_Ns := k_B = 1.380620000 × 10-23, T = 300, q = 1.602190000 × 10-19, Ids = 1.2172
```

$$\times 10^{-9} N_p, R_s = \frac{0.009200000000 N_s}{N_p}, R_h = \frac{12.7 N_s}{N_p}, \eta = 1.13$$

$$V_{th} = 0.02585124111 N_s$$

(3.3.2)

```
> data_Ns_full := subs(Ns = 56,Np = 2, [% , %%]);
```

```
data_Ns_full := [ Vth = 1.447669502, kB = 1.380620000 × 10-23, T = 300, q
```

$$= 1.602190000 \times 10^{-19}, I_{ds} = 2.4344 \times 10^{-9}, R_s = 0.2576000000, R_h$$

$$= 355.6000000, \eta = 1.13]$$

(3.3.3)

```
> I_ph1 := subs(Np = 2,Np * 6.1);
```

$$I_{ph1} := 12.2$$

(3.3.4)

```
> Voc_num := evalf( subs( data_Ns_full,I_ph = I_ph1, Voc));
```

```
Isc_num := evalf( subs( data_Ns_full,I_ph = I_ph1, Isc));
```

$$Voc_num := 36.523249$$

$$Isc_num := 12.19116859$$

(3.3.5)

```
> Pow_vol:=V__pv->V__pv*Iout(V__pv);
```

```
diff(Pow_vol(V__pv),V__pv) = 0;
```

```
subs(data_Ns_full,I_ph = I_ph1,%);
```

```
V__pv_max := fsolve(%,V__pv);
```

```
I__pv_max := evalf( subs(data_Ns_full,I_ph = I_ph1,Iout  
(V__pv_max)) );
```

```
Pow_max := evalf( subs(data_Ns_full,I_ph = I_ph1,Pow_vol  
(V__pv_max)) );
```

$$Pow_vol := V_{pv} \mapsto V_{pv} \cdot Iout(V_{pv})$$

$$\begin{aligned}
& \frac{1}{(Rh + Rs) Rs} \left(- (Rh + Rs) \eta V_{th} \text{LambertW} \left(\frac{\left(\frac{I_{ds} Rs + I_{ph} Rs + V_{pv}}{(Rh + Rs) \eta V_{th}} \right) Rh}{(Rh + Rs) \eta V_{th}} \right) \right. \\
& \quad \left. + Rs (I_{ds} Rh + I_{ph} Rh - V_{pv}) \right) \\
& \quad V_{pv} \left(- \frac{Rh \text{LambertW} \left(\frac{\left(\frac{I_{ds} Rs + I_{ph} Rs + V_{pv}}{(Rh + Rs) \eta V_{th}} \right) Rh}{(Rh + Rs) \eta V_{th}} \right)}{1 + \text{LambertW} \left(\frac{\left(\frac{I_{ds} Rs + I_{ph} Rs + V_{pv}}{(Rh + Rs) \eta V_{th}} \right) Rh}{(Rh + Rs) \eta V_{th}} \right)} - Rs \right) \\
& \quad + \frac{\left(\frac{I_{ds} Rs Rh e}{(Rh + Rs) \eta V_{th}} \right)}{(Rh + Rs) Rs} = 0 \\
& -6.350413578 \text{LambertW} \left(3.830676137 \times 10^{-10} e^{1.919744038 + 0.6108543039 V_{pv}} \right) \\
& + 12.19116861 - 0.002810112810 V_{pv} + 0.01090882302 V_{pv} \left(\right. \\
& \quad \left. - \frac{355.6000000 \text{LambertW} \left(3.830676137 \times 10^{-10} e^{1.919744038 + 0.6108543039 V_{pv}} \right)}{1 + \text{LambertW} \left(3.830676137 \times 10^{-10} e^{1.919744038 + 0.6108543039 V_{pv}} \right)} \right. \\
& \quad \left. - 0.2576000000 \right) = 0
\end{aligned}$$

$$V_{pv_{\max}} := 28.95339440$$

$$I_{pv_{\max}} := 11.39824241$$

$$Pow_{\max} := 330.0178078 \quad (3.3.6)$$

Another way to determine the maximum power and the corresponding voltage :

$$\begin{aligned}
& > \text{MPP_vol} := \text{Optimization} : -\text{Maximize}(\text{subs}(\text{data_Ns_full}, I_{\text{ph}} = \\
& \quad I_{\text{ph1}}, \text{Pow_vol}(V_{\text{pv}})), \{0 \leq V_{\text{pv}}, V_{\text{pv}} \leq \text{Voc_num}\}); \\
& \quad \text{MPP_vol} := [330.017807675594725, [V_{\text{pv}} = 28.9533944028819]] \quad (3.3.7)
\end{aligned}$$


Power versus voltage

$$\begin{aligned}
& > \text{display}(\text{plot}(\text{Pow_max}, V_{\text{pv}} = 0.. \text{Voc_num}, \text{linestyle}=\text{dash}, \\
& \quad \text{color}=\text{"Red"}),
\end{aligned}$$

```

pointplot([V__pv__max, 0],[V__pv__max, Pow_max]],
linestyle=dash,color="Red",connect=true),
plot(subs(data_Ns_full,I__ph = I__ph1,Pow_vol(V__pv)
),V__pv = 0..Voc_num, thickness = 3, transparency = 0.25),
labels = ["V__pv (V)","(W)"],
size = [800,500])

```

 


Animate the effect of photo current variation vs voltage

```

> animate(plot,[subs(data_Ns_full,Pow_vol(V__pv)),V__pv = 0..
Voc_num],I__ph = 0..I__ph1,
thickness = 3, transparency = 0.25,
labels = ["V__pv (V)","(W)"],

```

```
size = [800,500])
```

 


I-V curve of a photovoltaic panel

```
> display( plot(I__pv__max, V__pv = 0..Voc_num,linestyle=dash,
color="Red",thickness=1),
            pointplot([[V__pv__max, 0],[V__pv__max, Isc_num]],
linestyle=dash,thickness=1,color="Red",connect=true),
            plot(subs(data_Ns_full,I__ph = I__ph1, Iout
(V__pv)),V__pv = 0..Voc_num,color=c_set[1],
            legend=typeset(I__ph,"=100%")),
            plot(subs(data_Ns_full,I__ph = I__ph1*0.5, Iout
(V__pv)),V__pv = 0..Voc_num,color=c_set[2],
```

```

        legend=typeset(I__ph,"=50%")),
        plot(subs(data_Ns_full,I__ph = I__ph1*0.25, Iout
(V__pv)),V__pv = 0..Voc_num, color=c_set[3],
        legend=typeset(I__ph,"=25%")),
        labels = ['V__pv (V)','I__pv (A)'],
        thickness= 3, transparency = 0.25,
        view = [0..40,0..13],
        size      = [800,500]);

```

 

▼ **1) Simulation with external load with voltage ramp for load**

Simulation with constant external load

In this simulation, it is explored the behaviour of a photovoltaic (PV) panel system connected to a constant load over a 24-hour period. The purpose of this study is to understand how different factors such as irradiance and load demand affect the performance of the PV panel throughout the day.

Equations of pannel connected to a constant load

```
> eqns := [I__pv(t) - Iout(V__pv(t)),
            V__pv(t) = Pow/I__pv(t)
            ]
```

```
:
<%>
```

$$I_{pv}(t) - \frac{-(Rh + Rs) \eta V_{th} \text{LambertW} \left(\frac{I_{ds} Rs Rh e}{(Rh + Rs) \eta V_{th}} \right) \dots}{(Rh + Rs) Rs} \quad (4.1.1)$$

$$V_{pv}(t) = \frac{Pow}{I_{pv}(t)} \quad \dots$$

```
> #sol := op(solve(eqns,[I__pv(t),V__pv(t)]))
> [I__pv(t),V__pv(t)];
x2y := {seq(%[i] = op(0,%[i]),i=1..nops(%))};
```

$$x2y := \{I_{pv}(t), V_{pv}(t)\} \quad (4.1.2)$$

Simple case with constant Solar induced current $I_{ph} = 6$ and fixed value of Power request ($Pow = [40, 60, 80, 100]$)

```
> # Power set to 40 W
sol := fsolve(convert(subs(data_Ns_full,I__ph = 6, Pow = 40,
x2y, eqns),set),subs( x2y, {I__pv(t),V__pv(t)}));
sol := {I_pv = 5.976849671, V_pv = 6.692488886} \quad (4.1.3)
```

```
> # Power set to 60 W
sol := fsolve(convert(subs(data_Ns_full,I__ph = 6, Pow = 60,
x2y, eqns),set),subs( x2y, {I__pv(t),V__pv(t)}));
sol := {I_pv = 5.967399136, V_pv = 10.05463161} \quad (4.1.4)
```

```
> # Power set to 80 W
sol := fsolve(convert(subs(data_Ns_full,I__ph = 6, Pow = 80,
x2y, eqns),set),subs( x2y, {I__pv(t),V__pv(t)}));
sol := {I_pv = 5.957900949, V_pv = 13.42754784} \quad (4.1.5)
```

```
> # Power set to 100 W
```

```
sol := fsolve(convert(subs(data_Ns_full,I_ph = 6, Pow = 100,
x2y, eqns),set),subs( x2y, {I_pv(t),V_pv(t)}));
sol := {Ipv = 5.948233542, Vpv = 16.81171381} (4.1.6)
```

Simulation with costant load and Solar Irradiance modelled as a piecewise sinusoidal function


> Model the solar Irradiance I_r as a sinusoidal funtion with a peak at 12:17

```
I_r := t -> piecewise(t < 6, 0.01*t, t < 19, sin(t/4-1.5)
+0.1, 0);
```

```
# Plot Pow over a day
```

```
plot(I_r(t), t = 0 .. 24, title = "Solar Irradiation", labels
= ["Time (h)", "Current (A)"]);
```
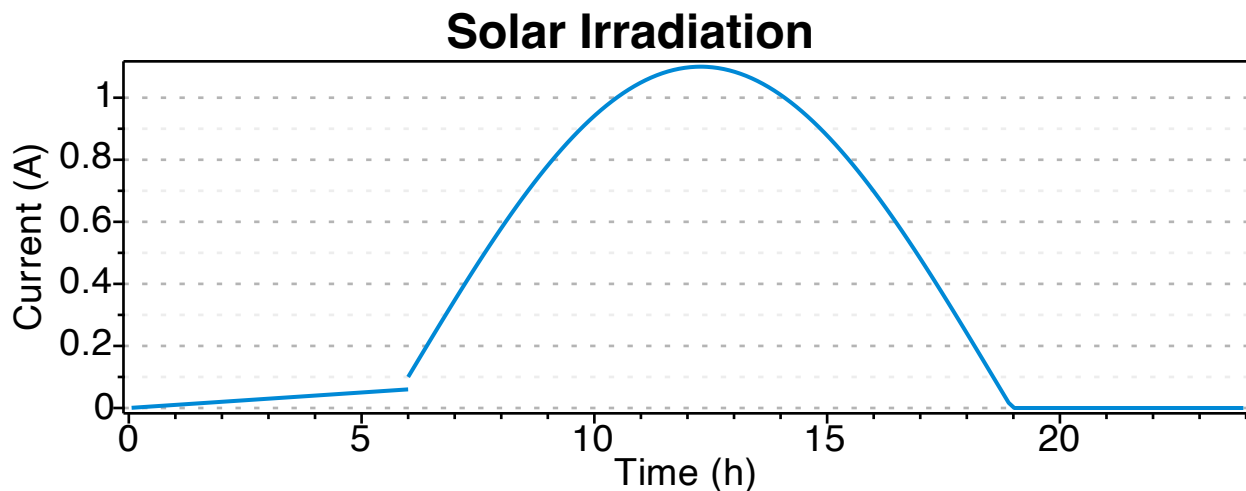
$$I_r := t \mapsto \begin{cases} 0.01 \cdot t & t < 6 \\ \sin\left(\frac{t}{4} - 1.5\right) + 0.1 & t < 19 \\ 0 & \text{otherwise} \end{cases}$$



Compute the maximum solar peak

```
> maximize(I_r(t),t=1..24,location);
1.100000000, {[t= 12.28318531}, 1.100000000]} (4.1.7)
```

> Constant Power requested modelled as a piecewise function


```
Pow_cons := t -> piecewise(t < 8, 0, t < 18, 40, 0);
```

```
#Plot Pow over a day
```

```
plot(Pow_cons(t), t = 0 .. 24, title = "Power Generation
Profile", labels = ["Time (h)", "Power (W)"]);
```

$$Pow_{cons} := t \mapsto \begin{cases} 0 & t < 8 \\ 40 & t < 18 \\ 0 & otherwise \end{cases}$$

Power Generation Profile

 

In this simulation, it is explored the behavior of a photovoltaic (PV) panel system connected to a constant load over a 24-hour period. The purpose of this study is to understand how different factors such as irradiance and load demand affect the performance of the PV panel system throughout the day.

Using the following code, the result from the previous iteration are considered at the iteration of fsolve.

```
> Ns := 100:
   Tf := 24:

   T_VEC := [seq(Tf/Ns*i, i=0..Ns)]:

   equations := subs(V__pv(t) = V_pv, I__pv(t) = I_pv, eval({
       I__pv(t) = Iout(V__pv(t)),
       V__pv(t) = Pow/I__pv(t)
   })):

   # Define the variable set for the solver
   vars:= {V_pv,I_pv}:

> tmp := fsolve(subs(data_Ns_full, t=T_VEC[1], I__ph = 7*800*
   I__r(0)/1000,Pow=Pow__cons(0),equations),vars):
   subs(data_Ns_full,I_ph = 9*800*I__r(0)/1000, t=T_VEC[1],eqns)
   :
```



```
sol := Matrix(1..Ns, 1..4, fill=0): # creates a matrix full of zeroes
```

```
> for k from 1 to Ns do
;
tmp := fsolve(subs(data_Ns_full, t=T_VEC[k], I_ph = 7*800*
I_r(T_VEC[k])/1000, Pow=Pow_cons(T_VEC[k]), equations), tmp):
sol[k,1..4] := (subs(t=T_VEC[k], tmp, <t,V_pv,I_pv,(V_pv*
I_pv)>)):

```

```
end:
```


```
sol:
pointp1 := pointplot(sol[1..-1,1],sol[1..-1,2],connect=true,
color=red, symbolsize=20,view=[default, 0..26],title =
"Voltage", labels = ["Time (h)", "V_pv (V)"]):
pointp2 := pointplot(sol[1..-1,1],sol[1..-1,3],connect=true,
color=blue, symbolsize=20,view=[default, 0..12],title =
"Current", labels = ["Time (h)", "I_pv (A)"]):

```


```
> line1 := plot(V_pv_max, x = 0..24, color = "red", linestyle
= dash, legend = "Max value with 100%power"):
line2 := plot(I_pv_max, x = 0..24, color = "blue", linestyle
= dash, legend = "Max value with 100%power"):
```

```
display(pointp1,line1,size = [600, 400]);
display(pointp2,line2,size = [600, 400]);
```

Voltage

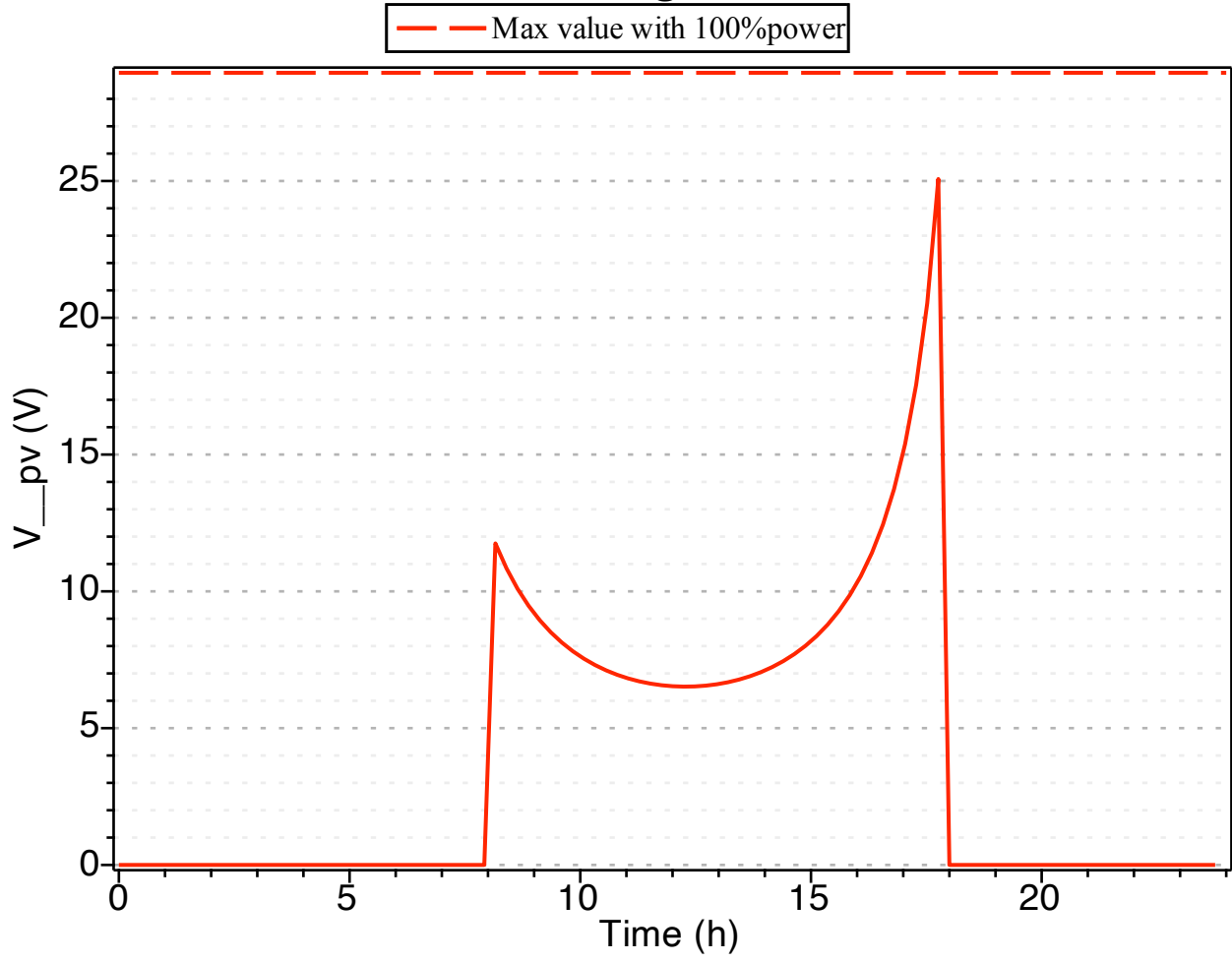

Current

 


In the following plot it is display the Power generated by the solar panel (multiplying the voltage times the current) obtaining the same the Load requested defined in the piecewise function "Pow_cons"

```
> pointp3 := pointplot(sol[1..-1,1],sol[1..-1,4],connect=true,  
  color=red, symbolsize=20,view=[default, 0..80],title = "Power  
  Generated", labels = ["Time (h)", "W"]):
```

```
line3 := plot(Pow_max, x = 0..24, color = "blue", linestyle =  
  dash, legend = "Max value with 100%power"):
```

```
display(pointp3,line3,size = [600, 400]);
```

Power Generated

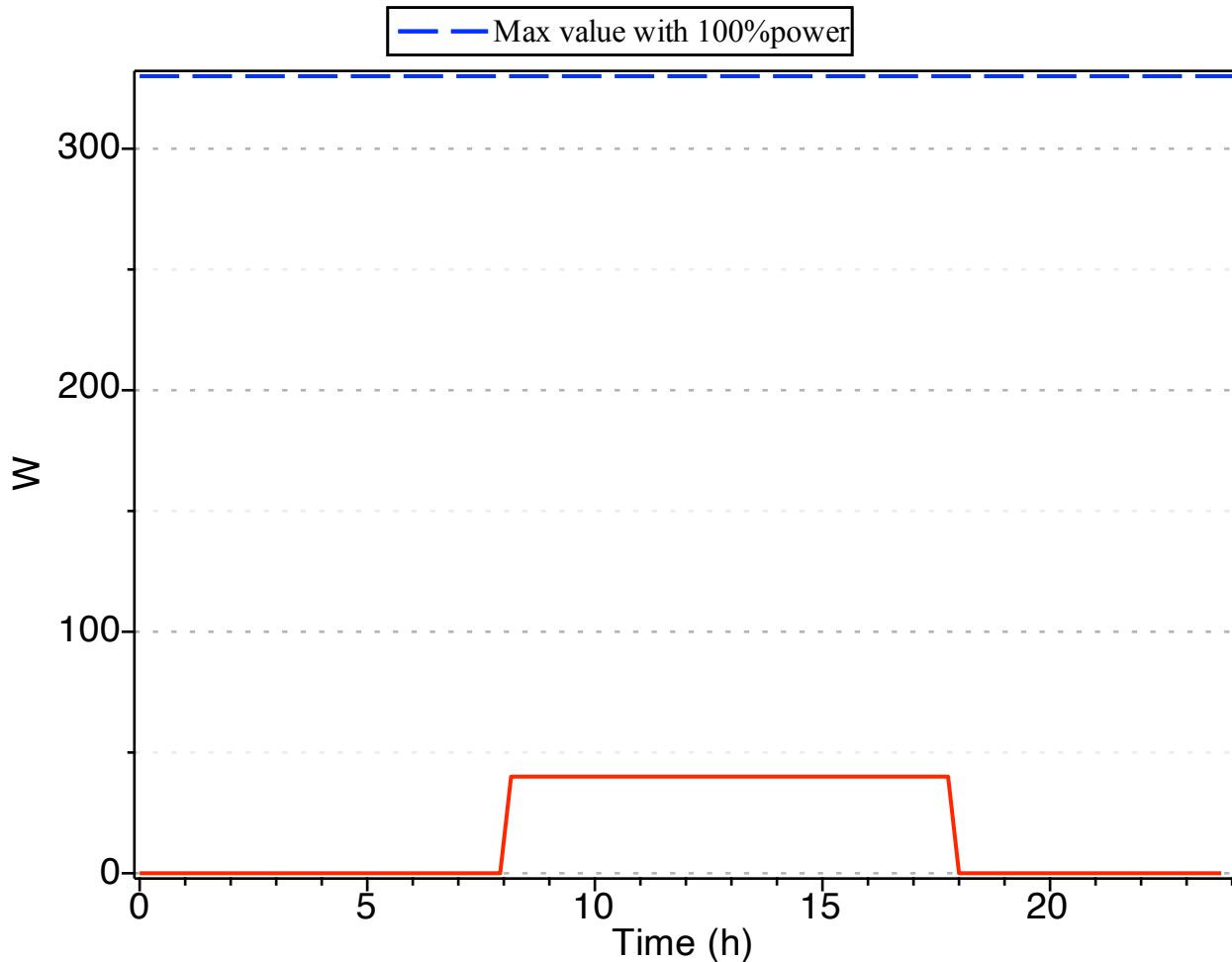

Simulation with various time law of the external load

[Define the time varying Power modelled as a piecewise function


```
> Pow := t -> piecewise(0.4*(t < 7, 0, t < 8, 90*(t-7), t < 12,
    32 + 7 * t, t < 16, 132 - 50 * sin(t/2 - 12), t < 17, 90-90*
    (t-16), 0));
```

#Plot Pow over a day

```
plot(Pow(t), t = 0 .. 24, title = "Power Requested Profile",
    labels = ["Time (h)", "Power (Watts)"]);
```

$$Pow := t \mapsto \begin{cases} 0.4 \cdot \begin{cases} t < 7, 0, t < 8, 90 \cdot t - 630, t < 12, 32 + 7 \cdot t, t < 16, 132 - 50 \cdot \sin\left(\frac{t}{2} - 12\right), t < 17, 90 - 90 \cdot (t - 16), 0 \end{cases} \end{cases}$$

Power Requested Profile

 

The procedure to solve the system in the different hours during the day

```
> Ns := 100:
   Tf := 24:

   T_VEC := [seq(Tf/Ns*i, i=0..Ns)]:

   equations := subs(V__pv(t) = V_pv, I__pv(t) = I_pv,eval({
       I__pv(t) = Iout(V__pv(t)),
       V__pv(t) = Pow/I__pv(t)
   })):

   # Define the variable set for the solver
   vars:= {V_pv,I_pv}:

> tmp := fsolve(subs(data_Ns_full, t=T_VEC[1], I__ph = 7*800*
   I__r(0)/1000,Pow=Pow(0),equations),vars):
   subs(data_Ns_full,I_ph = 7*800*I__r(0)/1000, t=T_VEC[1],eqns)
   :

   sol := Matrix(1..Ns, 1..4, fill=0): # creates a matrix full of
   zeroes

> for k from 1 to Ns do
   ;
   tmp := fsolve(subs(data_Ns_full, t=T_VEC[k],I__ph = 7*800*
   I__r(T_VEC[k])/1000,Pow=Pow(T_VEC[k]),equations),tmp):
   sol[k,1..4] := (subs(t=T_VEC[k], tmp, <t,V_pv,I_pv,(V_pv*
   I_pv)>)):

```


```
end:
```

```
sol:
```


```
pointp1 := pointplot(sol[1..-1,1],sol[1..-1,2],connect=true,  
color=red, symbolsize=20,view=[default, 0..16],title =  
"Voltage", labels = ["Time (h)", "V_pv (V)"]):  
pointp2 := pointplot(sol[1..-1,1],sol[1..-1,3],connect=true,  
color=blue, symbolsize=20,view=[default, 0..12],title =  
"Current", labels = ["Time (h)", "I_pv (A)"]):
```

```
> line1 := plot(V_pv_max, x = 0..24, color = "red", linestyle  
= dash, legend = "Max value with 100%power"):  
line2 := plot(I_pv_max, x = 0..24, color = "blue", linestyle  
= dash, legend = "Max value with 100%power"):
```
 
```
display(pointp1,line1,size = [600, 400]);  
display(pointp2,line2,size = [600, 400]);
```



Current

 


In the following plot it is display the Power generated by the solar panel (multiplying the voltage times the current) obtaining the same the Load requested defined in the piecewise function "Pow"

```
> pointp3 := pointplot(sol[1..-1,1],sol[1..-1,4],connect=true,
  color=red, symbolsize=20,view=[default, 0..80],title = "Power
  Generated", labels = ["Time (h)", "W"]):
```

```
line3 := plot(Pow_max, x = 0..24, color = "blue", linestyle =
  dash, legend = "Max value with 100%power"):
```
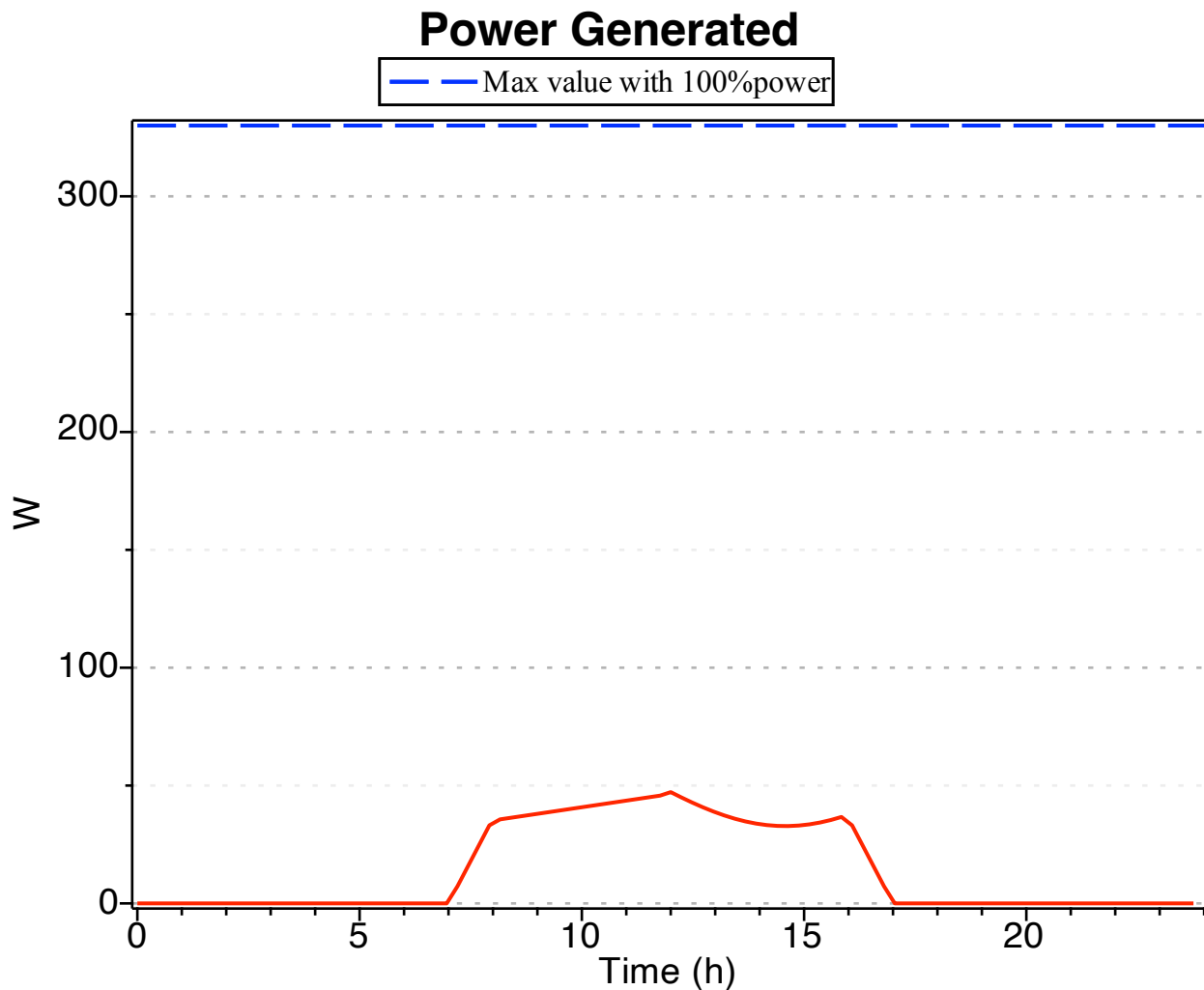
```
display(pointp3,line3,size = [600, 400]);
```



Another procedure to solve the system in the different hours during the day that do not considers the result from the previous iteration and it is less precise

```


> # Define the procedure
solpow := proc(n):
    fsolve(convert(subs(data_Ns_full, I__ph = 7*800*I__r(n)
/1000, Pow = 0.3*Pow(n), x2y, eqns), set), subs( x2y, {I__pv(t),
V__pv(t)}));
end proc:

> results := [seq([n, solpow(n)], n = 0..24)]:
> for i from 1 to 24 do
    results[i][2]:
    I__pv(i) := subs(%, I__pv):
    V__pv(i) := subs(%%, V__pv):
end do:

> with(plots):
pointplot([seq([r, V__pv(r)], r = 1..24)], style=line, color=
blue, symbolsize=20, view=[default, 0..20], title = "Voltage",
labels = ["Time (h)", "Vpv (V)"]);


```


Voltage

 

```
> with(plots):
pointplot([seq([r, I__pv(r)], r = 1..24)], style=line, color=
blue, symbolsize=20,view=[default, 0..12],title = "Current",
labels = ["Time (h)", "Ipv (V)"]);
```

Current

 

2) Simulation with external load and battery

Simulation with external load and battery connected (current constant)

In the simplified battery model provided in the paper: "Hybrid vehicle optimisation: lead acid battery modelling" the current I_0 is assumed to be constant for this reason in the next section the equations for the panel connected to the battery and a load are solved assuming the battery current constant, specifically $I_0 = 8$

```
> Ns := 100;
```

Tf := 24:

T_VEC := [seq(Tf/Ns*i, i=0..Ns)]:

equations__prova := {

$$\text{Pow_L} \quad V0_func(t, I_0) * (I_0 + Iout(V0_func(t, I_0))) =$$

$$\};$$

Define the variable set for the solver
vars2:= {Pow__L}:

$$equations_{prova} := \left\{ \frac{1}{1000.000000 + 1000.000000 e^{3.72444321 I_0 t}} \left(12623. + I_0 \left(\right. \right. \right. \quad (5.1.1)$$

$$-9718.07 e^{-0.00002247241511 t + 3.72444321 I_0 t} - 9718.07 e^{-0.00002247241511 t}$$

$$+ 9718.07 e^{3.72444321 I_0 t} + 9718.07 \ln(1 - 0.001694266338 I_0 t$$

$$-0.1437185100\,I_0\,t\max\big(0.,I_0\left(1.-1.\,\mathrm{e}^{-0.00002247241511\,t}\right)\big)^{0.64741}\bigg)+(12623.$$

$$-0.05413451899\,I_0^2\,t+(-92.06069999-314.8790363\,t)\,I_0\bigg)\,\mathrm{e}^{3.72444321\,I_0}$$

$$-0.05413451899\,I_0^2\,t+(-1984.39563-314.8790363\,t)\,I_0\bigg)\left(I_0\right.$$

$$+\frac{1}{(Rh+Rs)\,Rs}\left(-(Rh\right.$$

$$+Rs)$$

$$\eta\,V_{th}\,\mathrm{LambertW}\left(\frac{1}{(Rh+Rs)\,\eta\,V_{th}}\left(I_{ds}\,Rs\,Rh\right.$$

$$\frac{1}{(Rh+Rs)\,\eta\,V_{th}}\left(\left(I_{ds}\,Rs+I_{ph}\,Rs+\frac{1}{1000.000000+1000.000000\,\mathrm{e}^{3.72444321\,I_0}}\right)(12623.$$

$$\begin{aligned}
& + I_0 \left(-9718.07 e^{-0.00002247241511 t + 3.72444321 I_0} - 9718.07 e^{-0.00002247241511 t + 9718.07 e^{3.72444321 I_0}} \right. \\
& \left. + 9718.07 \right) \ln \left(1 - 0.001694266338 I_0 t - 0.1437185100 I_0 t \max \left(0, I_0 \left(1 - 1. e^{-0.00002247241511 t} \right)^{0.64741} \right) \right) \\
& + \left(12623. - 0.05413451899 I_0^2 t + (-92.06069999 - 314.8790363 t) I_0 \right) e^{3.72444321 I_0} - 0.05413451899 I_0^2 t + (\\
& -1984.39563 - 314.8790363 t) I_0 \left. \right) \left. \right) \left. \right) \left. \right) + R_s \left(I_{ds} R_h + I_{ph} R_h \right. \\
& - \frac{1}{1000.000000 + 1000.000000 e^{-0.00002247241511 t + 3.72444321 I_0} - 9718.07 e^{-0.00002247241511 t} \\
& + 9718.07 e^{3.72444321 I_0} + 9718.07} \ln \left(1 - 0.001694266338 I_0 t \right. \\
& - 0.1437185100 I_0 t \max \left(0, I_0 \left(1 - 1. e^{-0.00002247241511 t} \right)^{0.64741} \right) + \left(12623. \right. \\
& - 0.05413451899 I_0^2 t + (-92.06069999 - 314.8790363 t) I_0 \left. \right) e^{3.72444321 I_0} \\
& \left. - 0.05413451899 I_0^2 t + (-1984.39563 - 314.8790363 t) I_0 \right) \left. \right) \left. \right) \left. \right) = Pow_L \}
\end{aligned}$$

```

> tmp := fsolve(subs(data_Ns_full, t=T_VEC[1], I__ph = 7*800*
I__r(0)/1000, I__0=8, equations_prova), vars2):
sol := Matrix(1..Ns, 1..6, fill=0): # creates a matrix full of
zeroes

```

```

> for k from 1 to Ns do

```

```

    tmp := fsolve(subs(data_Ns_full, t=T_VEC[k], I__ph = 7*800*
I__r(k)/1000, I__0=8, equations_prova), tmp):
    sol[k, 1..6] := (subs(t=T_VEC[k], tmp, <t, Pow__L, V0__func
(T_VEC[k], 8), subs(data_Ns_full, t=T_VEC[k], I__ph = 7*800*
I__r(k)/1000, I__0=8, Iout(V0__func(t, I__0)))>)):
end:
#print(sol):

```

```

> pointp1 := pointplot(sol[1..-9, 1], sol[1..-9, 2], connect=true,

```

```

color=blue, symbolsize=20,view=[0..6,0..100 ],title = "Power
Generated", labels = ["Time (min)","W"]):
pointp2 := pointplot(sol[1..-1,1],sol[1..-1,4],connect=true,
color=blue, symbolsize=20,view=[0..6,0..10 ],title = "Current
(Output Solar Panel)", labels = ["Time (min)","A"]):
pointp3 := semilogplot(sol[1..30,1],sol[1..30,3],color=blue,
symbolsize=20,view=[default, default],title = "Voltage
(Battery)", labels = ["Time-log (min)","V"]):


```

This graph shows the power generated over time in a system where a battery is connected to an external load. It is evident that the power consistently decreases as the battery discharges. Additionally, there are localized increases in power when the current generated by the solar panel rises, reflecting the effects of increased solar irradiance. In this part of the simulation, time is modeled in minutes instead of hours to clearly demonstrate the impact of the solar panel on the battery, which discharges within minutes.

```

> display(pointp1,size = [600, 400]);


```

 

Output current of the solar panel considering the irradiance modelled in minutes instead of hours.
This is done to illustrate the effect of the effect of the solar panel and the Ceraolo battery at the same time connected together

```
> display(pointp2,size = [600, 400]);
```


Current (Output Solar Panel)

 

This graph shows the Ceraolo battery model discharge voltage over time, with time plotted on a logarithmic scale

```
> display(pointp3,size = [600, 400]);
```

Voltage (Battery)

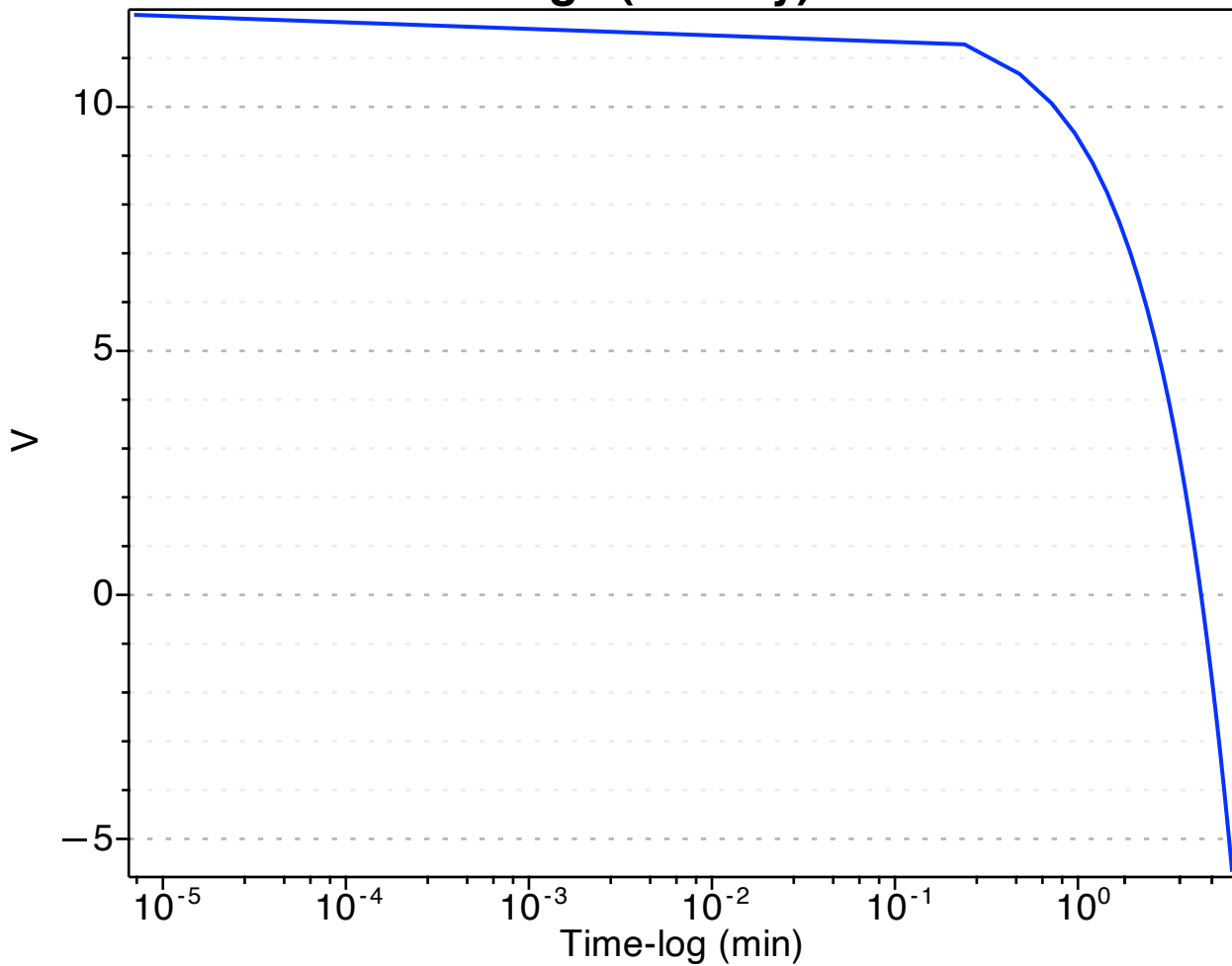

Simulation with constant external load and battery connected

Equations of pannel connected to a constant load with the procedure to solve the system in the different hours during the day.

In this simulation, it is explored the behaviour of a photovoltaic (PV) panel system connected to a constant load over a 24-hour period. The purpose of this study is to understand how different factors such as irradiance and load demand affect the performance of the PV panel and the connected battery system throughout the day.

```
> Ns := 100:
  Tf := 24:
```

```
  T_VEC := [seq(Tf/Ns*i, i=0..Ns)]:
```



```

equations__2 := subs(I__pv(t) = I_pv,eval({
    V0__func(t*60,I__0)-V__L, # times 60 to
transform the battery voltage low in hours
    Vout(I__pv(t))-V__L,
    V__L*(I__0+I__pv(t))=Pow__L
}));

```

```

# Define the variable set for the solver
vars2:= {I__0,I_pv,V__L}:

```

$$equations_2 := \left\{ \frac{1}{1000.000000 + 1000.000000 e^{3.72444321 I_0 t}} \left(12623. + I_0 \left(\right. \right. \right. \quad (5.2.1)$$

$$\left. -9718.07 e^{-0.001348344907 t + 3.72444321 I_0 t} - 9718.07 e^{-0.001348344907 t} \right.$$

$$\left. + 9718.07 e^{3.72444321 I_0 t} + 9718.07 \right) \ln \left(1. - 0.1016559803 I_0 t \right.$$

$$\left. - 8.623110600 I_0 t \max \left(0., I_0 \left(1. - 1. e^{-0.001348344907 t} \right) \right)^{0.64741} \right) + \left(12623. \right.$$

$$\left. - 3.248071139 I_0^2 t + \left(-92.06069999 - 18892.74218 t \right) I_0 \right) e^{3.72444321 I_0 t}$$

$$\left. - 3.248071139 I_0^2 t + \left(-1984.39563 - 18892.74218 t \right) I_0 \right) - V_L,$$

$$- \text{LambertW} \left(\frac{\frac{R h \left(I_{ds} - I_{pv} + I_{ph} \right)}{\eta V_{th}}}{\frac{I_{ds} R h e}{\eta V_{th}}} \right) \eta V_{th} + \left(-R h - R s \right) I_{pv} + \left(I_{ds} \right.$$

$$\left. \begin{aligned} &+ I_{ph}) Rh - V_L, V_L (I_0 + I_{pv}) = Pow_L \end{aligned} \right\}$$

```
> tmp := fsolve(subs(data_Ns_full,t=T__VEC[1],I__ph = 7*800*I__r
(0)/1000,Pow__L=0.3*Pow__cons(0),equations__2),vars2);
```

$$tmp := \{I_0 = 137.1160550, I_{pv} = 1.663567043 \times 10^{-19}, V_L = 0.\} \quad (5.2.2)$$

```
> subs(data_Ns_full,I_ph = 7*800*I__r(0)/1000, t=T__VEC[1],
equations__2):
```

```
sol := Matrix(1..Ns, 1..5, fill=0): # creates a matrix full of
zeroes
```

```
for k from 2 to Ns do
```


```
tmp := fsolve(subs(data_Ns_full, t=T__VEC[k],I__ph = 7*800*
I__r(T__VEC[k])/1000,Pow__L=0.3*Pow__cons(T__VEC[k]),
equations__2),tmp):
```

```
sol[k,1..5] := (subs(t=T__VEC[k], tmp, <t,I__0+I_pv,V__L,
(I_pv+I__0)*V__L>)):
```

```
end:
```


```
> sol:
pointp1 := pointplot(sol[1..-1,1],sol[1..-1,3],connect=true,
color=red, symbolsize=20,view=[default, 0..12],title =
"Voltage", labels = ["Time (h)", "V"]):
pointp2 := pointplot(sol[1..-1,1],sol[1..-1,2],connect=true,
color=blue, symbolsize=20,view=[default, 0..20],title =
"Current", labels = ["Time (h)","A"]):
```
 
```
display(pointp1,size = [600, 400]);
```



In the following plot it is possible to see a spike in the current due to the battery connected to model
 
```
> display(pointp2,size = [600, 400]);
```




In the following plot it is display the Power generated by the solar panel (multiplying the voltage times the current) obtaining the same the Load requested defined in the piecewise function "Pow_cons"

```
> pointp3 := pointplot(sol[1..-1,1],sol[1..-1,4],connect=true,
  color=red, symbolsize=20,view=[default, 0..60],title = "Power
  Generated", labels = ["Time (h)", "W"]):

#line3 := plot(Pow_max, x = 0..24, color = "blue", linestyle =
  dash, legend = "Max value with 100%power"):

display(pointp3,size = [600, 400]);
```

Power Generated

 

Simulation with various time law of the external load and battery connected

Equations of pannel connected to a time varying load with the procedure to solve the system in the different hours during the day

In this simulation, it is explored the behaviour of a photovoltaic (PV) panel system connected to a time-varying load over a 24-hour period. The purpose of this study is to understand how different factors such as irradiance and load demand affect the performance of the PV panel and the connected battery system throughout the day.

```
> Ns := 100:
   Tf := 24:
```

```
T_VEC := [seq(Tf/Ns*i, i=0..Ns)]:
```

```
equations_2 := subs(I_pv(t) = I_pv,eval({
```

```

V0__func(t*60,I__0)-V__L,
Vout(I__pv(t))-V__L,
V__L*(I__0+I__pv(t))=Pow__L
}));

```

```

# Define the variable set for the solver
vars2:= {I__0,I__pv,V__L}:

```

$$equations_2 := \left\{ \frac{1}{1000.000000 + 1000.000000 e^{\frac{3.72444321 I_0}{-0.001348344907 t + 3.72444321 I_0}}} \left(12623. + I_0 \left(\right. \right. \right. \quad (5.3.1)$$

$$\left. -9718.07 e^{\frac{3.72444321 I_0}{-0.001348344907 t + 3.72444321 I_0}} - 9718.07 e^{-0.001348344907 t} \right.$$

$$\left. + 9718.07 e^{\frac{3.72444321 I_0}{-0.001348344907 t + 3.72444321 I_0}} + 9718.07 \right) \ln \left(1. - 0.1016559803 I_0 t \right.$$

$$\left. - 8.623110600 I_0 t \max \left(0., I_0 \left(1. - 1. e^{-0.001348344907 t} \right) \right)^{0.64741} \right) + \left(12623. \right.$$

$$\left. - 3.248071139 I_0^2 t + \left(-92.06069999 - 18892.74218 t \right) I_0 \right) e^{\frac{3.72444321 I_0}{-0.001348344907 t + 3.72444321 I_0}}$$

$$\left. - 3.248071139 I_0^2 t + \left(-1984.39563 - 18892.74218 t \right) I_0 \right) - V_L,$$

$$- \text{LambertW} \left(\frac{\frac{R h \left(\frac{I_{ds} - I_{pv} + I_{ph}}{\eta V_{th}} \right)}{I_{ds} R h e}}{\eta V_{th}} \right) \eta V_{th} + \left(-R h - R_s \right) I_{pv} + \left(I_{ds} \right.$$

$$\left. \begin{aligned} &+ I_{ph}) Rh - V_L, V_L (I_0 + I_{pv}) = Pow_L \end{aligned} \right\}$$

```
> tmp := fsolve(subs(data_Ns_full, t=T_VEC[1], I_ph = 7*800*
I_r(0)/1000, Pow_L=Pow(0), equations__2), vars2);
```

$$tmp := \{I_0 = 137.1160550, I_{pv} = 1.663567043 \times 10^{-19}, V_L = 0.\} \quad (5.3.2)$$

```
> subs(data_Ns_full, I_ph = 7*800*I_r(0)/1000, t=T_VEC[1],
equations__2):
```

```
sol := Matrix(1..Ns, 1..5, fill=0): # creates a matrix full of
zeroes
```

```
for k from 2 to Ns do
```


```
tmp := fsolve(subs(data_Ns_full, t=T_VEC[k], I_ph = 7*800*
I_r(T_VEC[k])/1000, Pow_L=Pow(T_VEC[k]), equations__2), tmp):
sol[k, 1..5] := (subs(t=T_VEC[k], tmp, <t, I_0+I_pv, V_L,
(I_pv+I_0)*V_L>)):
```

```
end:
```

```
> sol:
```


```
> pointp1 := pointplot(sol[1..-1, 1], sol[1..-1, 3], connect=true,
color=red, symbolsize=20, view=[default, 0..12], title =
"Voltage", labels = ["Time (h)", "V"]):
pointp2 := pointplot(sol[1..-1, 1], sol[1..-1, 2], connect=true,
color=blue, symbolsize=20, view=[default, 0..10], title =
"Current", labels = ["Time (h)", "A"]):
```
 
```
display(pointp1, size = [600, 400]);
```



In the following plot it is possible to see a spike in the current due to the battery connected to model

```
> display(pointp2,size = [600, 400]);
```

 In the following plot it is display the Power generated by the solar panel (multiplying the voltage times the current) obtaining the same the Load requested defined in the piecewise function "Pow"

```
> pointp3 := pointplot(sol[1..-1,1],sol[1..-1,4],connect=true,
  color=red, symbolsize=20,view=[default, 0..60],title = "Power
  Generated", labels = ["Time (h)", "W"]):

#line3 := plot(Pow_max, x = 0..24, color = "blue", linestyle =
  dash, legend = "Max value with 100%power"):

display(pointp3,size = [600, 400]);
```

Power Generated

